

MID Term Assessment

Md Bakhtiar Chowdhury

ID: 2121210061

Department: CSE

Semester: Summer 2023

Batch: 21th

Course Title: Digital Logic Design

Course Code: CSE 213

Submitted To:

Md. Shahin Khan

Lecturer, Dept. of CSE/CSIT

Victoria University of Bangladesh

Submission Date: 10 October 2023

Answer to the question no 1

a)
$$A + A'B$$

= $A + A \cdot B$
= $A \cdot 4 + A \cdot B$
= $A \cdot (1 + B)$
= $A \cdot (8 + 1)$
= $A \cdot 4$
= $A \cdot 4$

b)
$$A'B' + AB$$

$$= (A+B)' + AB'$$
Demotigan's theorem
$$(A+B)' = A'B'$$

$$A'B' = A+B$$
we can first apply be morgan theorem.
$$A'B' = (A' + B')'$$
then apply demotigan theorem.
$$(A' + B')' = A + B$$

c)
$$(A+B)$$
 $(A+C) = A^2 + AC + AB + BC$
Distributivity law
 $(A+B)$ $(C+D) = AC + AD + BC + BD$.

Then we can expand each of the products in paratheses $(A+B)(A+c) = A^2 + Ac + AB + Bc$ Ans.

d) (A+B+C+D) '=

De morgan's theorem states that the component of a sum of the product of the complements and vice vorsa, therefore the component of the expression is A'B'C'D' Ams.

e) (ABCD)' = A'+B'+C'+D'De 'morrgan's theotrem. (A+B+C+D)' = A'B'C'D'

De morigion theorem state that the component of a sum of the product of the components and vice versa. Therefore, the complement of the expression ABCD is the sum of the complements of A, B, C and D.

Answer to the question no 2

Absorption Law

Idempotent law

Applying those identities we get.

= A

therefore, the simplified form of the function is A

muth table

A B		B	A'B+AB	A'B'+ AB	(A'B+A'B)+(A'B+AB)	A
	0	0	0	0	0	0
•	0	1	0	1		0
	1	0	1	Ø	1	1
	•	1	1	1		1

The function can be simplied using the following boolean algebra

commutative law: A+B = B+A

Idempotent law: A+A=A

Absorption Law: A+AB=A

Applying these identifies, we get

$$= A'c(B'+B) + A(B'c'+Bc)$$

$$= A'C(1) + A(C')$$

Next we can use the distributive law to distribute the c'term


Over the A and Alterms

Therefore the simplified form of the function is e'

A	В	C A'B'C+ A'BC'+ AB'C'+ABC			
0	AND THE RESERVE TO SERVE THE PROPERTY OF THE P			1	
0	0	1	0	0	
0 1 0		0	0	1	
0	1	1	1	0	
1 0		0	0 0	1	
1	0	1	0	0	
1	1	0	0	1	
1	1	1	1	0	

Answer to the question no 3

4)

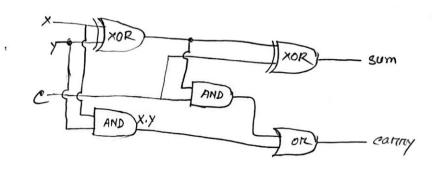

Function for

sum = x'y'C + x'yC' + xy'C' + xyC

omd


canny = xy +xc+yc

Amswer to the question NO 3(b)

Answer :-

$$F = (A+B'+C)' \times NOR(A+D)$$

 $F = A'+B+C' \times NOR(A+D)$

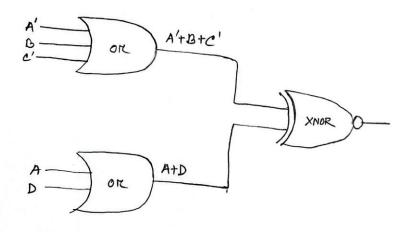

Answere to the question NO 4

Answer:-

Trouth table

A	В	Cin	sum	cout
0	0	0	0	0
.0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
	T.		1	

>>>>END<