

Name : Fardouse Iomat Jahan Rumpa

ID : 2219170041

Dept : B.Sc in CSE

course title : Digital Logic Design

Course code : CSE 213

Semester : Summer 2023

Ans to the que NO 01

Ⓐ  $A + A'B = ?$

In absorption law,

$$A + A'B = A$$

So,  $A + A'B$  is equal to  $A$  (Ans)

Ⓑ  $A'B' + AB = ?$

Use distributive law,

$$A'B' + AB = (A' + A)B'$$

Now,  $(A' + A)$  is always equal to 1

$$\text{So, } A'B' + AB = (1)B'$$

$$= B' \quad (\text{Ans})$$

Ⓒ  $(A+B)(A+C) = ?$

Use distribution law,

$$(A+B)(A+C) = A(A+C) + B(A+C)$$

$$= A(A+C)$$

$$= AA + AC$$

$$= A + A \times C$$

$$B(A+C) = BA + BC = AB + BC$$

So, expect is

$$(A+B)(A+C) = (A+AC) + (AB+BC)$$

# Apply  $\{(A+A) = A\}$  and  $(A+A^c) = A$  in Boolean Algebra

$$(A+AC) + (AB+BC) = A + (AB+BC)$$

So,  $(A+B)(A+C)$  simplify to

$$A + (AB+BC)$$

①  $(A+B+C+D)'$  = ?

Apply De Morgan's theorem.

$$(A+B+C+D)' = A^c B^c C^c D^c$$

So,  $(A+B+C+D)'$  is equal to  $A^c B^c C^c D^c$

②  $(ABCD)'$  = ?

Now,  $(ABCD) = A' + B' + C' + D'$

Ans to the Qus NO: 02 (b)

Ans:  $A'B'c' + A'BC + AB'c + ABC$  Step 1  $A'B$  is common to terms 1 and 2 so

$$A'B(c' + c) = A'B \text{ as } c' + c = 1$$

We now have

$$A'B + AB'c + ABC$$

Step 2 note that  $AC$  is common to terms 2 and 3 so,

$$A'B + AC(B' + B) \text{ recall that } B' + B = 1$$

Answer then becomes  $A'B + AC$ .

Ans to the Qus NO: 02 (a)

Ans: The given expression seems to have a closing parenthesis mismatch. Assuming the expression is  $(A'B + A'B') + (A'B' + AB)$ , let's simplify

using Boolean algebra laws:

1.  $A'B + A'B' = A'$  (Absorption Law)

2.  $A'B' + AB = B + A'B'$  (Absorption Law)



Now, the simplified expression becomes,

$$F = A'B + B + A'B'$$

If you meant a different expression or if there was a mistake in the input, please provide the correct expression for further assistance.

Ans to the Ques NO: 03


$$(a) \{ \overline{(x+y)+e} \} + \{ \overline{(x+y)c+xy} \}$$

Ans:

⇒ The function for the given circuit.

$$(b) F = (A + B' + c)' \times \text{NOR}(A + D)$$

Ans:

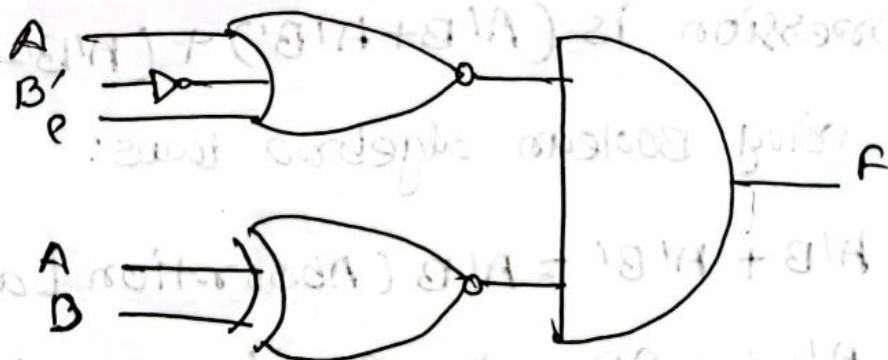

Ans to the Qus No: 04

Ans: Truth Table for the functions.

$$\{ \overline{(x+y)+c} \} + \{ (\overline{x+y})c + xy \} \quad [\text{from 3a}]$$

x	y	c	$\bar{x}$	$\bar{y}$	$\bar{c}$	$\bar{x+y}$	$\overline{(x+y)+c}$	$(\overline{x+y})c$	xy	$(\overline{x+y})c+xy$	$\{ \overline{(x+y)+c} \} + \{ (\overline{x+y})c + xy \}$
0	0	0	1	1	1	1	1	0	0	0	1
0	0	1	1	1	0	1	1	1	0	1	1
0	1	0	1	0	1	1	0	0	0	0	1
0	1	1	1	0	0	1	1	1	0	1	1
1	0	0	0	1	1	1	0	0	0	0	1
1	0	1	0	1	0	1	1	1	0	1	1
1	1	0	0	0	1	0	0	0	1	1	1
1	1	1	0	0	0	0	0	0	1	1	1