

Name - Md. Rakib Hasan.

ID - 2216080021

Course - Digital Logic Design.

Code - CSE - 213

Answer to the Question No - 1

(a)  $A + A'B = ?$

Inboscption law

$$A + A'B = A$$

So,  $A + A'B$  is equal to A Ans

(b)  $A'B' + AB = ?$

Use distributive law

$$A'B' + AB = (A' + A)B'$$

Now  $(A' + A)$  is always equal to 1.

$$\text{So, } A'B' + AB = (1)B'$$

$$= B' \text{ Ans}$$

(c)  $(A+B)(A+C) = ?$

Use distribution law

$$(A+B)(A+C) = A(A+C) + B(A+C)$$

$$= A(A+C)$$

$$= AA + AC$$

$$= A + A \cdot C$$

$$= B(A+C) = BA + BC = AB + BC$$

So,  $(A+B)(A+C) = (A+Ac) + (AB+Bc)$

# Apply  $\{(A+A) = A\}$  &  $\{(A+A)C = A\}$  in Boolean Algebra.

$(A+Ac) + (AB+Bc) = A + (AB+Bc)$

So  $(A+B)(A+C)$  simplify to  $A + (AB+Bc)$

$A + (AB+Bc)$

(d)

$(A+B+C+D)' = ?$

Apply De Morgan's theorem,

$(A+B+C+D)' = A'B'C'D'$

So  $(A+B+C+D)'$  is equal to  $A'B'C'D'$

(e)

$(ABCD)' = ?$

Here  $(ABCD) = A'+B'+C'+D'$

Answer to the question - 2

10/10/2023 20:25

$$\begin{aligned} \textcircled{b} & A'Bc + A'Be' + AB'e + ABC \\ &= A'Bc + ABc + A'Bc' + AB'e + ABC \quad \left( A'Bc = A'Bc' + A'Bc \right) \\ &= A'Bc + ABc + A'Be' + AB'e + ABc' + ABc \\ &= Bc(A'+A) + Bc'(A'+A) + AB(c'+c) \\ &= Bc + Bc' + AB' \end{aligned}$$

Hence, option (D)  $AB' + Bc + Bc'$  is the correct choice

Ans:  $(A'B + A'B) + (A'B' + AB)$  Step 1,  $A'B$  is Common

$= A'B + A'B$  to terms 1 and 2 so

$A'B(c'+c) = A'B$  as  $c'+c=1$

We know have,  $A'B + AB'c + ABc$

Step-2 not that  $AC$  is common to terms 2 and 3, so

$A'B + AC(B'+B)$  Recall that  $B'+B=1$

Answer them becomes  $A'B + AC$ .




Answer to the Question no - 3

(a)  $\left\{ \overline{(x+y)+c} \right\} + \left\{ \overline{(x+y)c+xy} \right\}$  Ans.

( $\Rightarrow$ ) The function for the given circuit.

(b)  $F = (A+B'+C)' \text{ XNOR } (A+D)$

Ans:

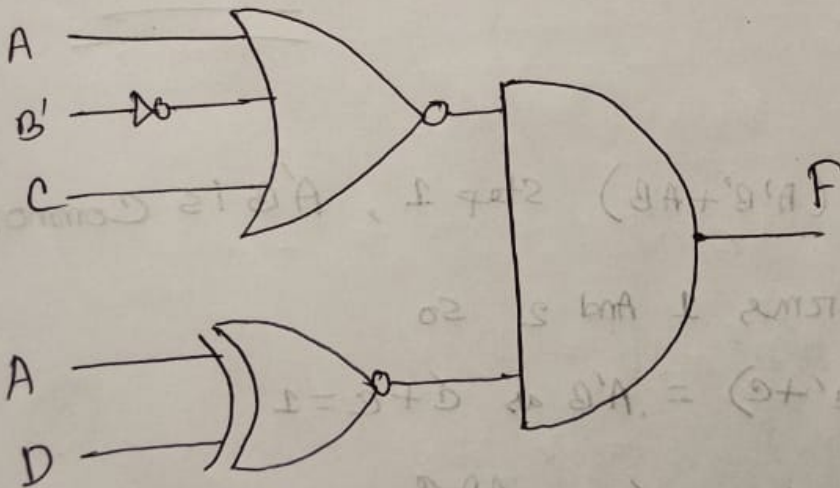

Answers to the Question - No - 4

Ans: Truth Table for the function:  $\{ \overline{(x+y)+c} \} + \{ (x+y)c + xy \}$   
 (from -3 @)

X	Y	C	$\bar{X}$	$\bar{Y}$	$\bar{C}$	$\overline{x+y}$	$\overline{x+y+c}$	$(x+y)c$	XY	$(x+y)c+xy$	$\overline{(x+y)+c} + \{ (x+y)c + xy \}$
0	0	0	1	1	1	1	1	0	0	0	1
0	0	1	1	1	0	1	1	1	0	1	1
0	1	0	1	0	1	1	1	0	0	0	1
0	1	1	1	0	0	1	1	1	0	1	1
1	0	0	0	1	1	1	1	0	0	0	1
1	0	1	0	1	0	1	1	1	0	1	1
1	1	0	0	0	1	0	1	0	1	<del>0</del> 1	1
1	1	1	0	0	0	0	0	0	1	1	1