

Victoria University of Bangladesh
Department of Computer Science & Engineering

Name: Ashit Kumar (Abir)

Student ID: 2221220011

Mid Assessment

Program: B.Sc in (CSE)

Semester: Fall - 2023

Batch: 22nd (Evening)

Course code: CSE-223

Course Title: Digital Electronics and pulse
Technique.

①

Ans to the ques No - 1(a)

In electronics, flip-flops and latches are circuits that have two stable states that store state information. A bistable multivibrator. The circuit can be made to change state by signals.

Example :-

This simple flip-flop circuit has set input(s) and a reset input(r). In this system, when you set 's' as active, the output Q would be high, and \bar{Q} would be low once the output is established - the wiring of the circuit is maintained until "s" or "R" go high, or power is turned off.

Ans to the ques No - 1(b)

Two types of Sequential circuits:

(a) Asynchronous Sequential circuit -

① Depends upon the input signal at any instant of time and their change order.

② They have better performance but hard to design.

(b) Synchronous Sequential circuit:

① Defined from the knowledge of its signals at discrete instants of time.

② much easier to design.

②


- ③ Synchronized by a periodic train of clock pulses.

Ans to the ques No - 2(a)

Controlled Latches:

Using JK flip-flop Controlled latches are drawn on the opposite page -

JK latch

 

(3)


We can show a characteristic table to show detail about JK latch. Here is the characteristic table -

Q	J	K	Q (H1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Diagram Table:- Characteristic Table.

Ans to the ques No- 2 (b)

 Here is drawn the master slave SR flip-flop (negative edge triggered) -




(9)

Ans to the ques No-3(a)

- A) The mealy model: The outputs are functions of both the present state and inputs.
- ① The outputs may change if the inputs change during the clock pulse period.
- ② The outputs may have momentary false values unless the inputs are synchronized with the clocks.
- B) The moore model: The outputs are functions of the present state only
- ① The outputs are synchronous with the clocks.

Ans to the ques No-3-(b)

A) Mealy State machine:

 

figone:- Block diagram of mealy machine

(b)

following the block diagram here is a table of mealy machine mealy


Present State		IP	Next State	O/P
A	B	X	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
1	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	1	1	0	1
1	1	0	1	0

Ans to the ques no - 3 (b)

(c)

More State Diagram:

State/Output

 

state Redection

④ Segmentation Circuit analysis —

Circuit diagram \rightarrow state table (on state diagram)

(6)

- ② Sequential circuit design -
State diagram (state table) \rightarrow circuit diagram
- ③ Redundant state may exist in a state diagram
(on table)
- ④ By eliminating them \rightarrow reduce the #
of logic gates and flip-flops.