

Victoria University of Bangladesh
Program:- B.Sc in CSIT

Dept:- CSE

Semester:- Spring-2024

Course code:- DLD 213

Course title:- Digital Logic Design

Name:- Husnat Jahan Tanshe

ID:- 2520200011

Batch:- 20

Final Submission

①


②

Ans to the Q no - 1(a)

*) Demux is a one-to-many circuit, which is exactly the opposite to the multiplexer. With the use of a Demultiplexer, data from one input can be passed to one of the many output data lines.

- *) 1 data input (D)
- *) 2 select lines (S1 and S0)
- *) 4 outputs (A0, A1, B0, B1)

Logic diagram:-

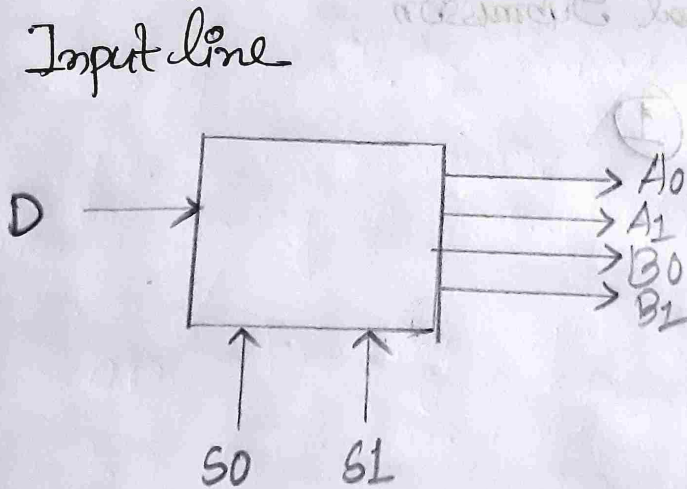

Truth table:

For a 2-to-4 demultiplexer, the select lines S1 and S0 determine which output line (A0, A1, B0, B1) the output (D) will be routed to

(2)

S1	S0	A0	A1	B0	B2
0	0	D/1	0	0	0
0	1	0	D/1	0	0
1	0	0	0	D/1	0
1	1	0	0	0	D/1

Explanation:-

- ① When $S1=0$ and $S0=0$, the input D is routed to Y0.
- ② When $S1=0$ and $S0=1$, the input D is routed to Y1.
- ③ When $S1=1$ and $S0=0$, the input D is routed to Y2.
- ④ When $S1=1$ and $S0=1$, the input D is routed to Y3.

In each case, only one ~~input~~ output is active (carrying the value of D), while the others are inactive (set to 0).

Ans to the Q no - 1(b)

An encoder is a combinational circuit that converts one of its 2^n inputs to a binary code of n bits.

Octal to Binary encoder:- An octal to binary encoder has 8 inputs and 3 outputs.

③

Truth table:-

Octal Input	Binary Input
000	000
001	001
010	010
011	011
100	100
101	101
110	110
111	111

Limitations of Octal to Binary Encoder:-

1. Single Input Activation: Only one input should be active at any given time, which may not always be practical.

2. Priority Encoding Required: In practical applications, if more than one input is active, a priority encoder is needed to determine which input to encode.

3. Complexity Increases with Input: - As the number of inputs increases, the complexity of the encoder also increases.


(4)

Ans to the Qno 2(a)

A decoder is a combinational circuit that converts n binary inputs to 2^n unique outputs.

3-to-8 line decoder: A 3-to-8 line decoder takes 3 input lines and decodes them into one of 8 outputs.

Logic Diagram:-

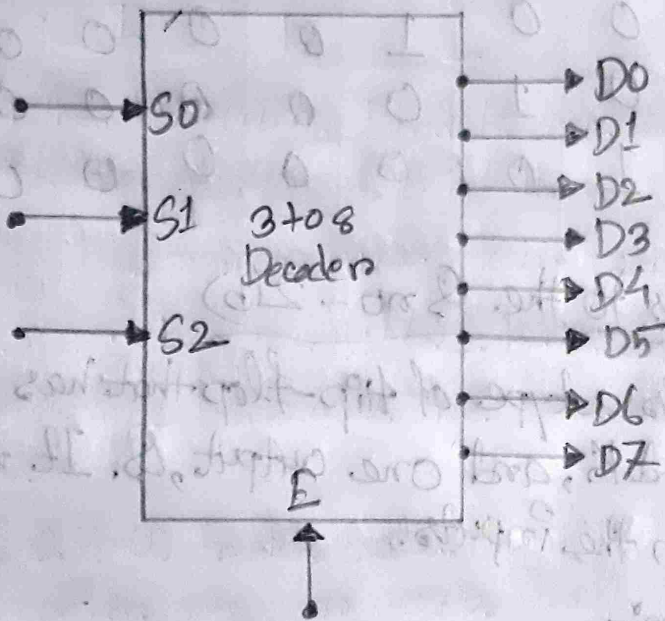

(5)


Truth table:

Inputs				Outputs							
S0	S1	S2	E	D0	D1	D2	D3	D4	D5	D6	D7
x	x	x	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	0	0	0	1	0
0	1	0	1	0	0	0	0	0	1	0	0
0	1	1	1	0	0	0	0	1	0	0	0
1	0	0	1	0	0	0	1	0	0	0	0
1	0	1	1	0	0	1	0	0	0	0	0
1	1	0	1	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Ans to the Q no - 2(b)

A JK flip-flop is a type of flip-flop that has two inputs, labeled J and K, and one output, Q. It toggles its output based on the inputs.

Logic Diagram:-

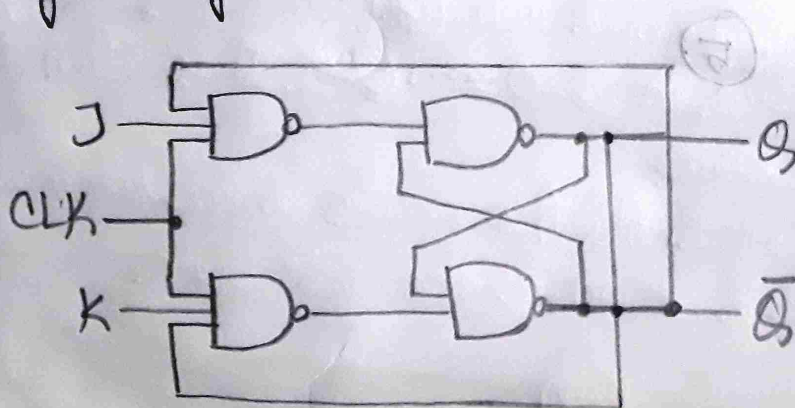

(6)

Truth Table

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

In the diagram, J and K are inputs, Q is the output, and Q' is the complement of the output.

JK flip flop comprises four possible combinations of inputs; $J=0, K=0$; $J=0, K=1$; $J=1, K=0$; and $J=1, K=1$. These input combinations determine the behaviour of flip flop and its output.

② $J=0, K=0$: In this state, flip flop retains its preceding state. It neither sets nor resets itself, making it stable.

④ $J=0, K=1$: This input combination forces flip flop to reset, resulting in $Q=0$ and $Q=1$. It is often referred to as the "reset" state.

③ $J=1, K=0$: Here, flip flop resides in the set mode, causing $Q=1$ and $Q=0$. It is known as the "set" state.

⑦

① $J=K, K=1$: This combination toggles flip flop. If the previous state is $Q=0$, it switches to $Q=1$ and vice versa. This ~~p~~ makes it valuable for frequency division and data storage applications.

Characteristic Equation of JK Flip Flop

The characteristic equation of JK flip flop represents the relationship between the current state ($Q(t)$), the inputs (J and K), and the next state ($Q(t+1)$). Here is the characteristic of JK flip flop.

$$Q(t+1) = J\bar{Q}(t) + QK(t)$$

In this equation, the term $J\bar{Q}(t)$ represents the effect of the J input when it is in the set formation ($J=1$), and $K(t)$ represents the effect of the K input when it is reset ($K=0$). The term $QK(t)$ represents the effect of the K input when it is in the set form ($K=1$), and $\bar{Q}(t)$ represents the complement of the current state.

②

Ans to the Q no - 3(a)

Find the complement of the functions ~~F1~~ $F1 = x'y'z' + x'y'z'$ and $F2 = X(y'z' + yz')$ by applying De Morgan's theorem.

Complement of $F1$:

$$F1 = x'y'z' + x'y'z'$$

Applying De Morgan's theorem:

$$F1' = (x'y'z' + x'y'z')$$

$$= (x'y'z') \cdot (x'y'z')$$

$$= (x+y+z) \cdot (x+y+z')$$

Complement of $F2$:

$$F2 = X(y'z' + yz')$$

$$= X(y'z')$$

Applying De Morgan's theorem:

$$F2' = (X(y'z'))'$$

$$= X' + (y'z')$$

$$= X' + (y+z)$$

(9)

Ans to the Q no 3(b)

Decimal to Binary Conversion:

Decimal 41 in binary is 101001101.

Integer Quotient, Remainder, and Coefficient:

① Divided 41 by 2:

$$\square 41/2 = 20 \text{ quotient, remainder } 1$$

$$\square 20/2 = 10 \text{ quotient, remainder } 0$$

$$\square 10/2 = 5 \text{ quotient, remainder } 0$$

$$\square 5/2 = 2 \text{ quotient, remainder } 1$$

$$\square 2/2 = 1 \text{ quotient, remainder } 0$$

$$\square 1/2 = 0 \text{ quotient, remainder } 1$$

So, the binary form of 41 is read from bottom to top, which is 101001101.

⑩